

# Remaining Topics

- Semiconductor Memory
  - Reference: ‘Analysis and Design of Digital Integrated Circuits’ by Hodges, Jackson, and Saleh
- Digital Logic using BJTs
- Layout

# Semiconductor Memories

# Classification

	<u>Volatile</u>	<u>Speed</u>	<u>Density</u>
SRAM	Yes	High	Moderate
DRAM	Yes	Moderate	High
ROM	No	High	Moderate
EPROM	No	Low	Low
Flash	No	Low	High
MRAM	No	High	Moderate
FeRAM	No	High	Moderate

# Classification

	<u>Volatile</u>	<u>Speed</u>	<u>Density</u>
→ SRAM	Yes	High	Moderate
→ DRAM	Yes	Moderate	High
ROM	No	High	Moderate
EPROM	No	Low	Low
→ Flash	No	Low	High
MRAM	No	High	Moderate
FeRAM	No	High	Moderate

# Memory Classification

## Stand Alone Memory

- DRAM, ROM, SRAM, FLASH, EPROM
- MRAM, FeRAM

## Embedded Memory

- SRAM for cache
- DRAM
- ROM

# Memory Market

## September 2006 Chip Sales Reached \$21.4 Billion

SAN JOSE, CA – November 16, 2006 – The Semiconductor Industry Association (SIA) today released its annual forecast of global semiconductor sales, projecting that the industry will continue to ride a strong wave of consumer demand for electronic products, driving sales to \$321 billion in 2009. The SIA forecast projects a compound annual growth rate of 9 percent for the forecast period, 2006-2009. Total worldwide microchip sales in 2005 amounted to \$227.5 billion.

MEMORY accounted for ~25% of the total market


DRAM sales are projected to be the fastest-growing segment

- Compound annual growth rate >14% in 2006-2009
- Sales especially strong for remainder of 2006 and in 2007 --> Vista OS

Sales of NAND flash are projected to grow at compound annual rate of 11% through 2009.

- Driven by replacement of hard drives; Laptop computers with pure NAND drives are projected to account for up to 25 percent of the laptop market by 2009

# Memory Market

 


Source: BCC, Incorporated

12/12/16


ECE445
 
## Historical Cost of Computer Memory and Storage





# AMD Athlon

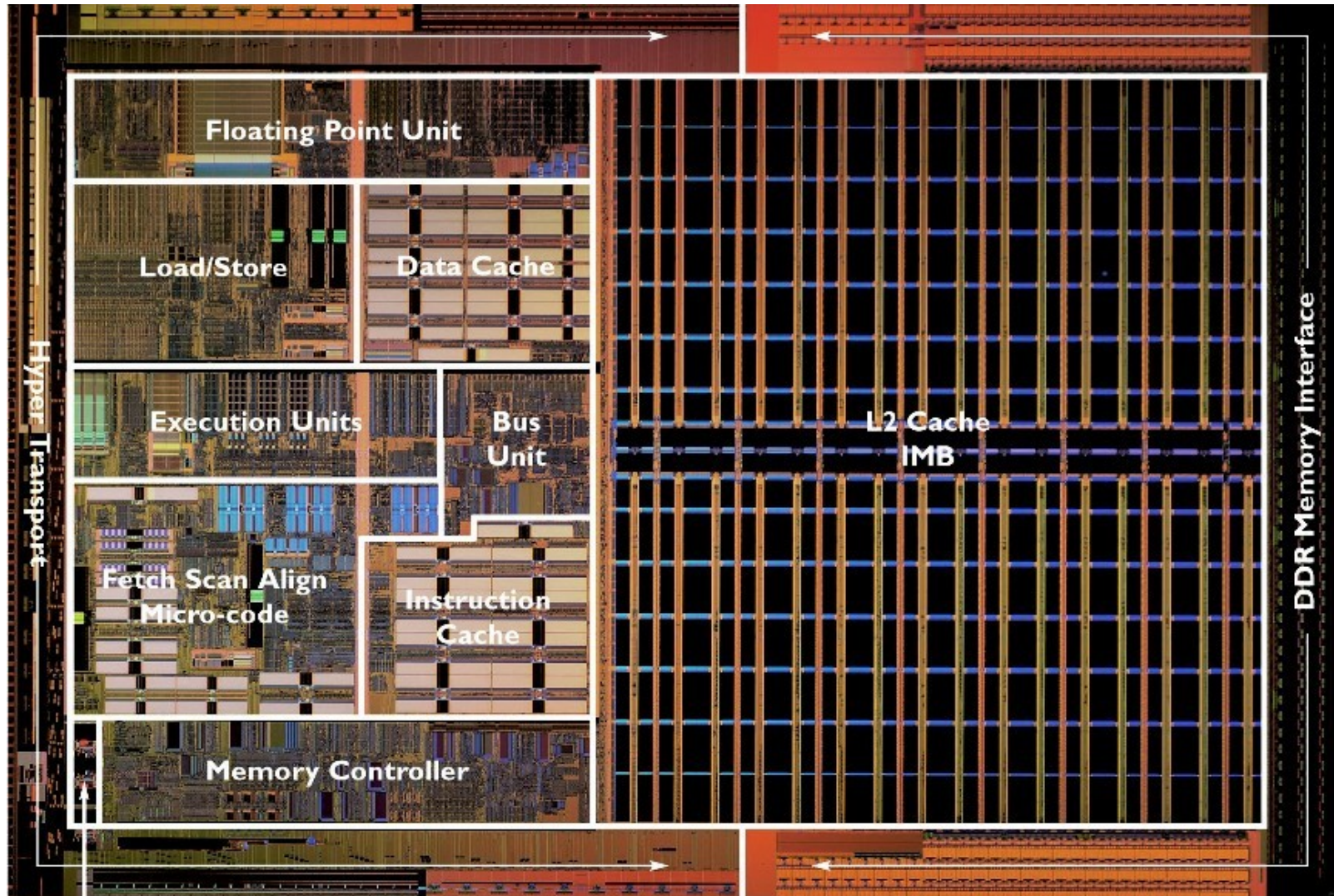



12/12/16

**Clock Generator**

ECE445



9

# AMD Dual-Core Athlon

  


# Memory Density

# Cell Size

 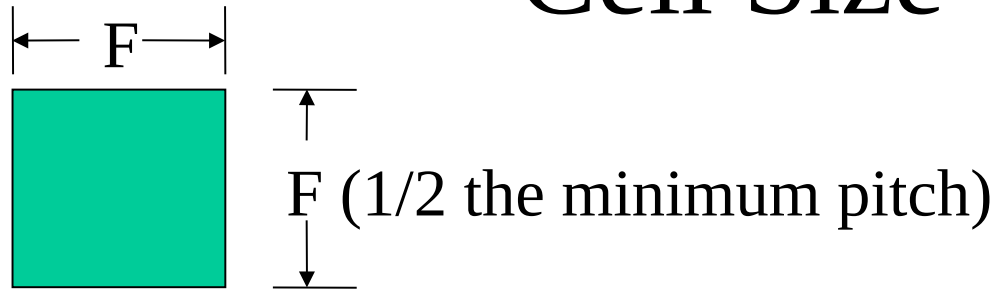


SRAM 6-T cell:  
40-100  $F^2$  cell

 DRAM 1-T, 1-C cell:  
5-10  $F^2$  cell; most common  $8F^2$  cell




# 1T 1R1C1 DRAM Cell

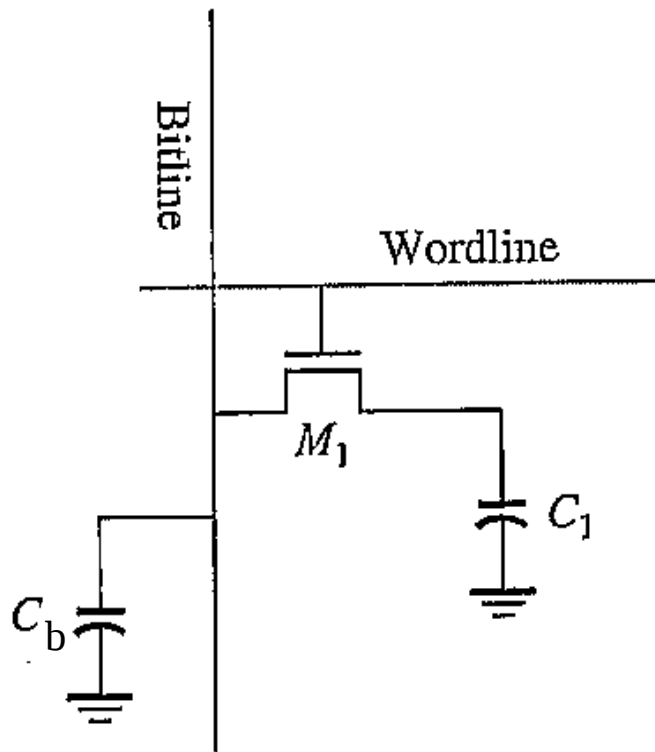




# 4Gb DRAM

 

# DRAM Trench Capacitor
 
## Extendability of Established Device Structures



# Redundancy

Redundancy is always used on standalone DRAMs and frequently for embedded DRAMs.

Implemented via on chip fuses in which fuses are blown either by a laser pulse or by an electrical pulse during wafer test.

Normally a few rows and columns of redundancy are offered on a large DRAM embedded macro. Smaller macros require less redundancy (or no redundancy)

Redundancy can also be implemented to some extent in the logic part of the circuits. To implement a spare decoder, for example, switches can be used that shift all decoder connections by one to bypass the faulty decoder.



# Memory Standards

Most memory standards are controlled by the **JEDEC** Solid State Technology Association (Once known as the **Joint Electron Device Engineering Council**). JEDEC is the semiconductor engineering standardization body of the Electronic Industries Alliance (EIA), a trade association that represents all areas of the electronics industry and was originally created in 1960 to cover the standardization of discrete semiconductor devices and later expanded in 1970 to include integrated circuits.

**JEDEC** does its work through its 48 committees/ subcommittees that are overseen by the **JEDEC** Board of Directors. Presently there are about 300 member companies in **JEDEC** including both manufacturers and users of semiconductor components and others allied to the field.

# DRAM Architecture

More than 10 Different Types of DRAM

Page Mode DRAM

Fast Page Mode DRAM

Extended Data Output DRAM

Burser Extended Data Output DRAM

Enhanced DRAM

Synchronous DRAM

PC100 Synchronous DRAM

Enhanced Synchronous DRAM

Double Data Rate DRAM

Direct Rambus DRAM

Synchronous Link DRAM

DRAM

FPM DRAM

EDO DRAM

BEDO DRAM

EDRAM

SDRAM

PC100 SDRAM

ESDRAM

DDR DRAM

DRDRAM

SLDRAM


# Memory Circuits

Memory Core                      - typically stores 1-bit  
   - can have multilevel cores)

## Peripheral Circuits


- row and column decoders
- sense amplifiers
- column precharge circuits
- data buffers
- read/write (R/W) circuits
- ...

# Typical Memory Organization

 


# 64 Kb RAM ( $2^8 \times 2^8$ )

$256 \times 256 = 65,536$  bits

 

# Timing Signals

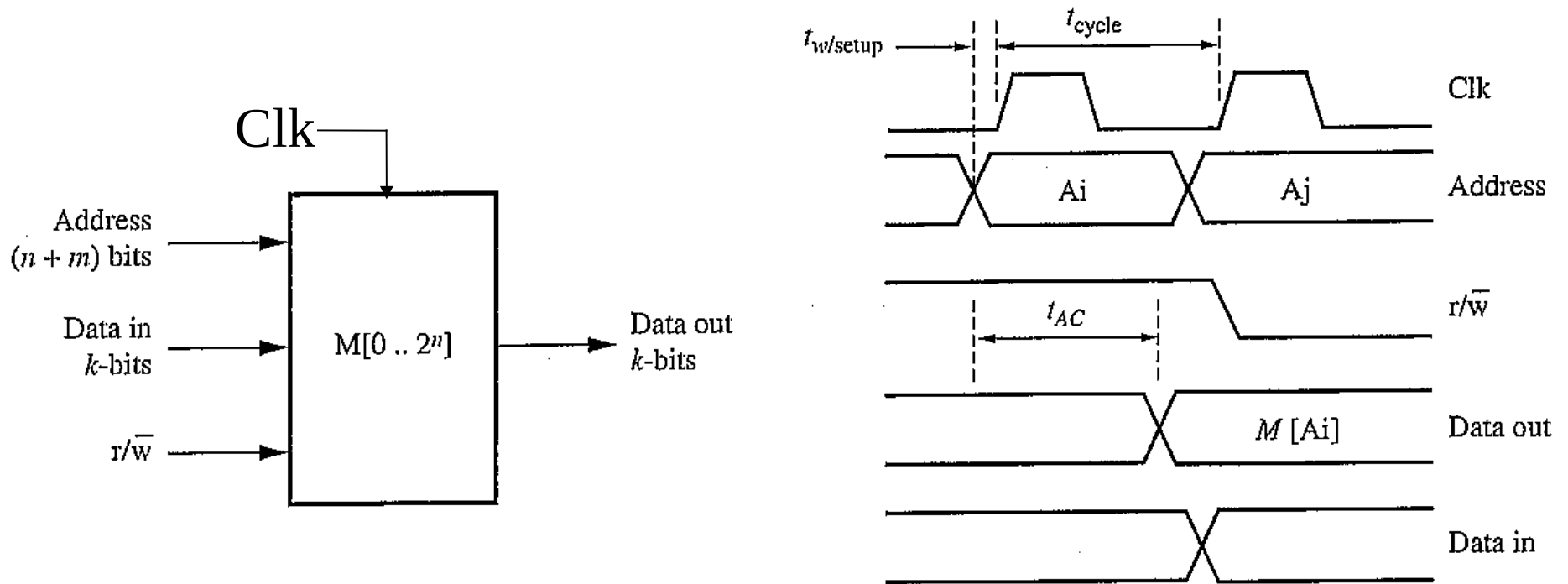


$t_{CYCLE}$  – minimum time to complete successive read or write operations


$t_{W/SETUP}$  – write setup time

$t_{AC}$  – read access time – delay from change in the address until data from that address are available at the output

# Row Decoder (n=2)

 

(a) AND-based decoder

 

(b) NOR-based decoder

# Cascade Decoder

An n-bit decoder  $\rightarrow 2^n$  logic gates each with n inputs

For n=6  $\rightarrow$  requires 64, 6-input NAND gates and 64 Inverters



To minimize delay caused by large series resistances  $\rightarrow$  cascade

- predecode stage
- final decode stage


Allows intermediate signals from the predecode stage to be reused by the final decoding stage




# Alternative 6-input NAND

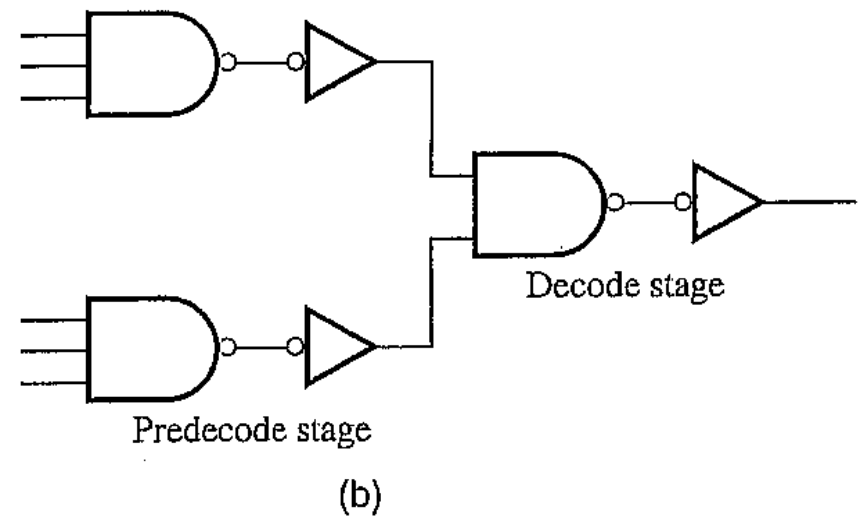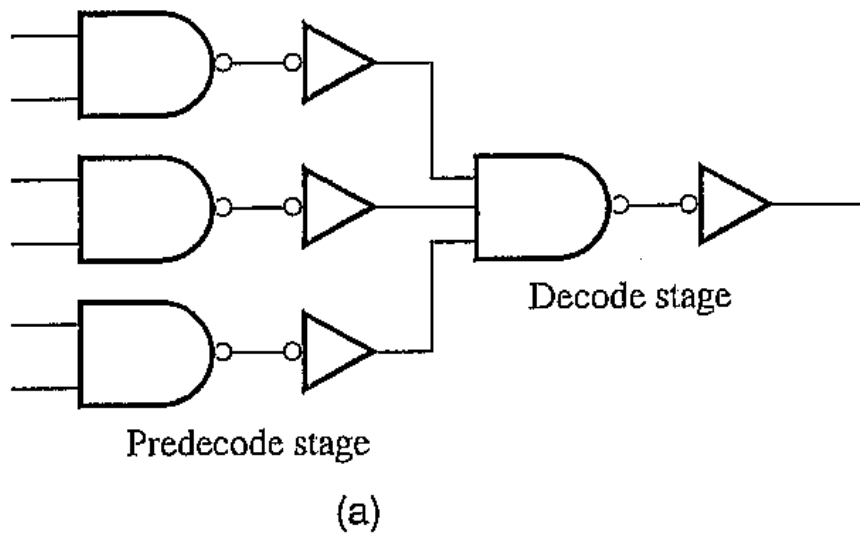

# Reuse of Intermediate Signals

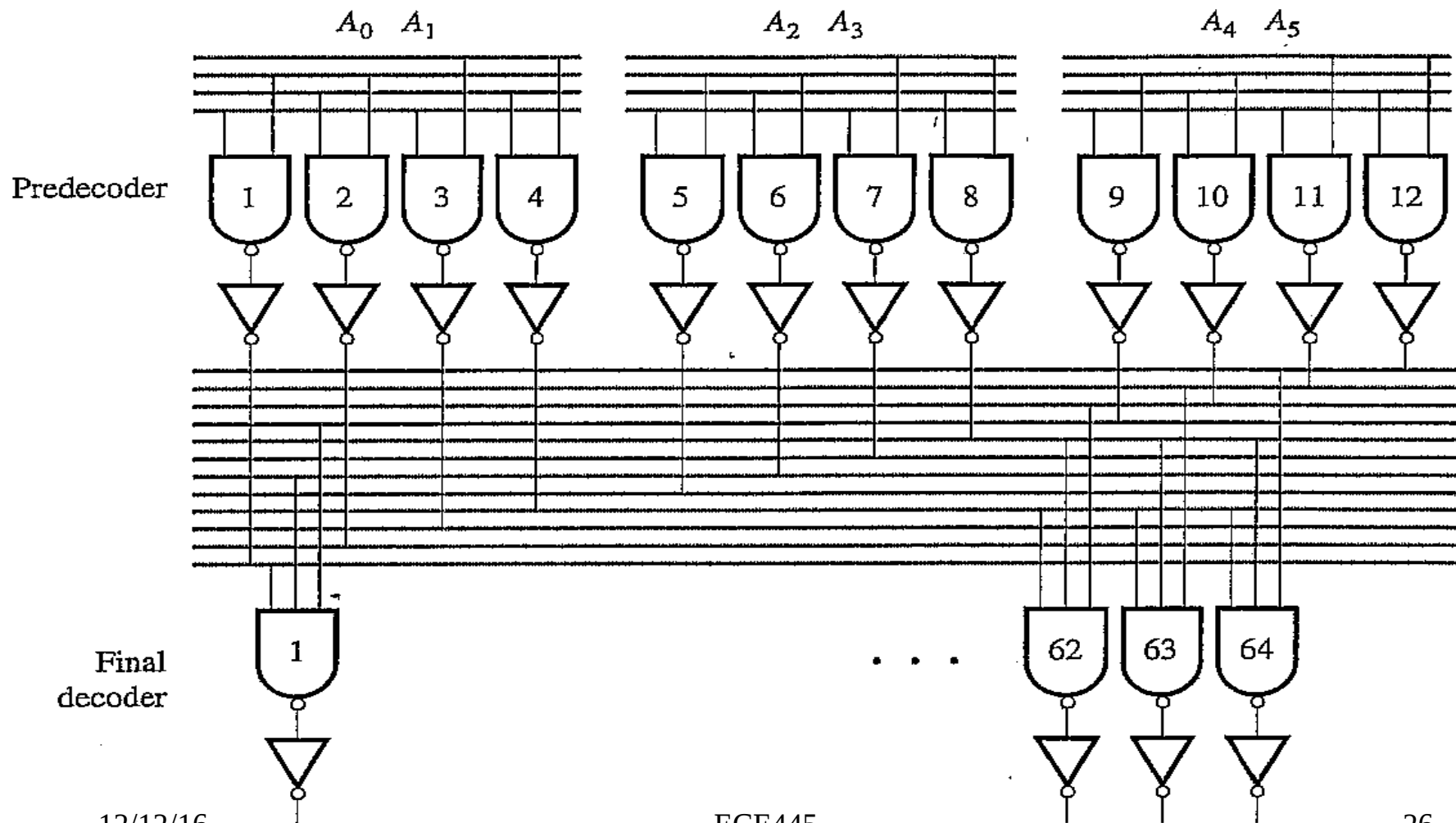

# Sizing Using Logical Effort

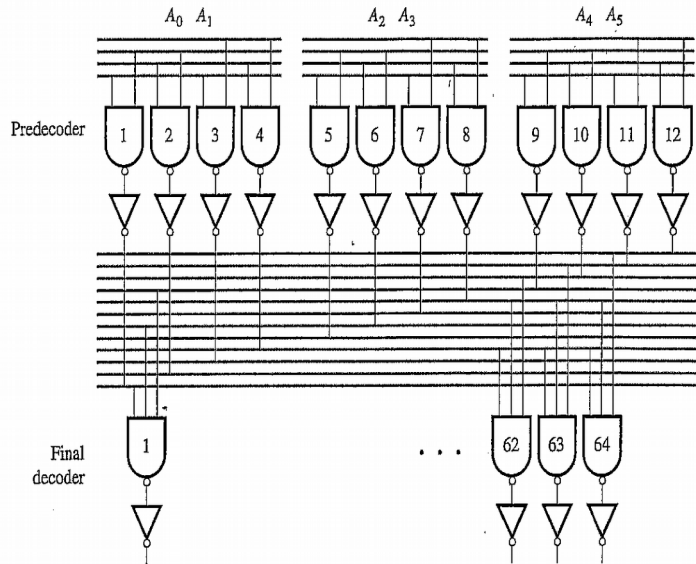

Size the decoder assuming:

- normalized output load = 1
- fan-out = 4


Work backwards from the output to the input:

- Normalized output has a size =
- Inverter input capacitance =
- The Logical Effort of the 3-input NAND =
- Input capacitance of 3-input NAND =
- Branching effort at output of predecoder =
- Input capacitance of the inverter =
- The 2-input NAND has an input capacitance =

## 12/12/16




# SRAM (Static RAM) Cell

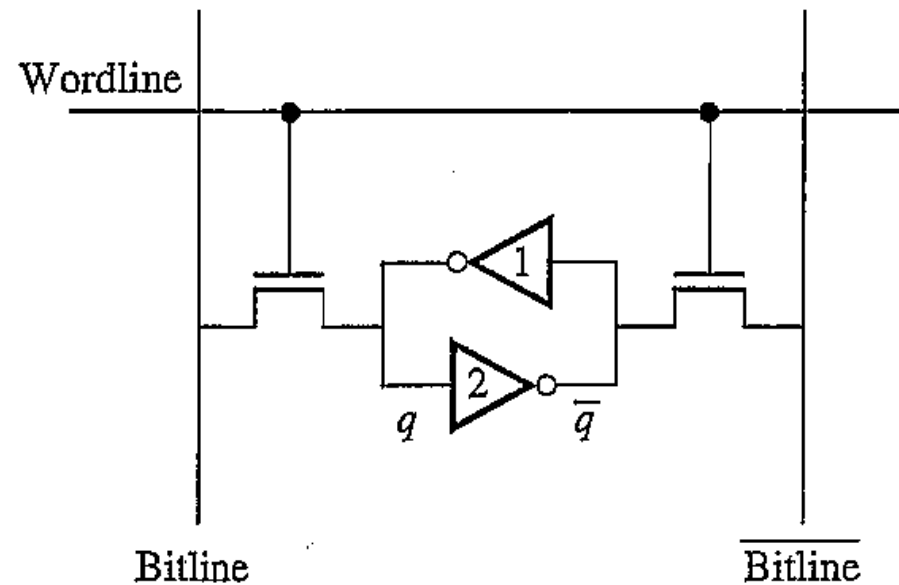


(a)

Basic SRAM Cell

# Voltage Transfer Characteristics

 

# 6-T Configuration

 

# Cell Design Considerations


1. Minimize Cell Area  $\leftrightarrow$  Increase cell density
  - replace load resistors (M5 and M6) with transistors
  - utilize TFTs for M5 and M6
  - reduce wasted area
2. Minimize static power  $\rightarrow$  Increase  $V_t$  and sub- $V_t$  slope
3. Differential bitlines  $\rightarrow$  improved noise immunity




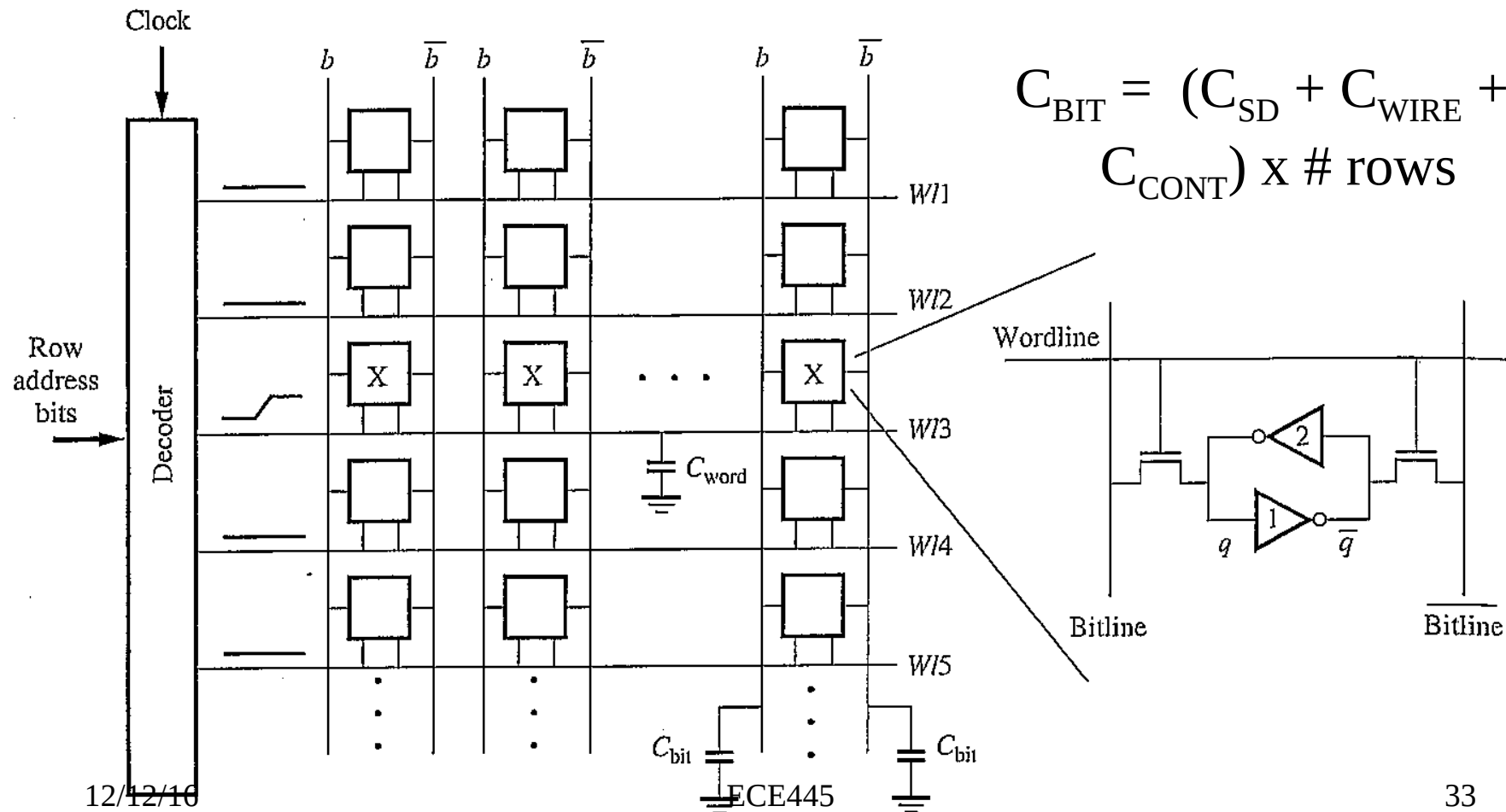
# SRAM Array (simplified)

$$C_{\text{WORD}} = 2 (C_G + C_{\text{WIRE}}) \times \# \text{ columns}$$

$$C_{\text{BIT}} = (C_{\text{SD}} + C_{\text{WIRE}} + C_{\text{CONT}}) \times \# \text{ rows}$$





# SRAM Read Operation

 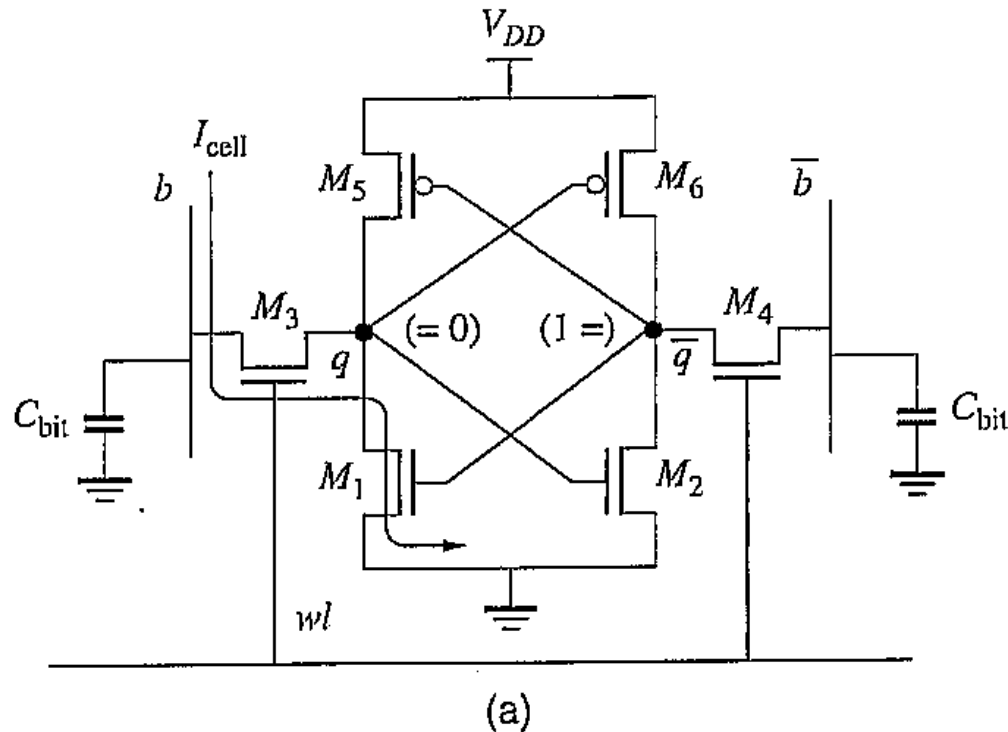

1. Precharge  $b, \bar{b}$  to  $V_{DD}$  column pull-up R
2. Turn on wordline to select row
3.  $C_{bit}$  slowly discharges on either  $b$  or  $\bar{b}$
4.  $b$  and  $\bar{b} \rightarrow$  sense amplifier

# SRAM Write Operation

  

1. Force either  $b$  or  $\bar{b}$  low
2. Turn on appropriate word line
3. Node  $q$  or  $\bar{q}$  is driven low causing the state to switch


# Transistor Sizing Guidelines

1. During read: need to ensure stored value is not disturbed – voltage can not drop below  $V_s$
2. Make conductance of M1, M2 greater than M3, M4
3. Need to supply enough  $I_{\text{CELL}}$  to discharge  $C_{\text{BIT}}$  sufficiently in 20-30% of a clock cycle
4. Can estimate  $I_{\text{CELL}}$

$$I_{\text{CELL}} = C_{\text{BIT}} \Delta V / \tau$$

5. During write: make conductance of M3, M4 greater than M5, M6

# Cell Layout

 

# SRAM Column I/O Circuitry

## Pre-charge (PC) circuitry

- used prior to a read or write operation to pull bit lines 'high'
- equalize  $b$  and  $b\bar{}$  potentials

## Address transition detection (ADT) circuitry to generate PC signal

- triggered by any transition of the address inputs


## Column decoder – multiplexer

## Read and Write circuitry

- R/W selection circuit
- sense amplifiers for read operation
- write drivers for write operation

# Column Pull-up Circuitry

Dynamic Logic Precharge P

 


12/12/16

(a)

seudo-NMOS Precharge


Important to  
equalize bitline  
voltage before  
reads

 

ECE445

(b)

NMOS Saturated Enhancement Load

 


(c)

39


# Address Transition Detection (ADT)

## Generate the PC signal

 




# Column Decoder / Multiplexer

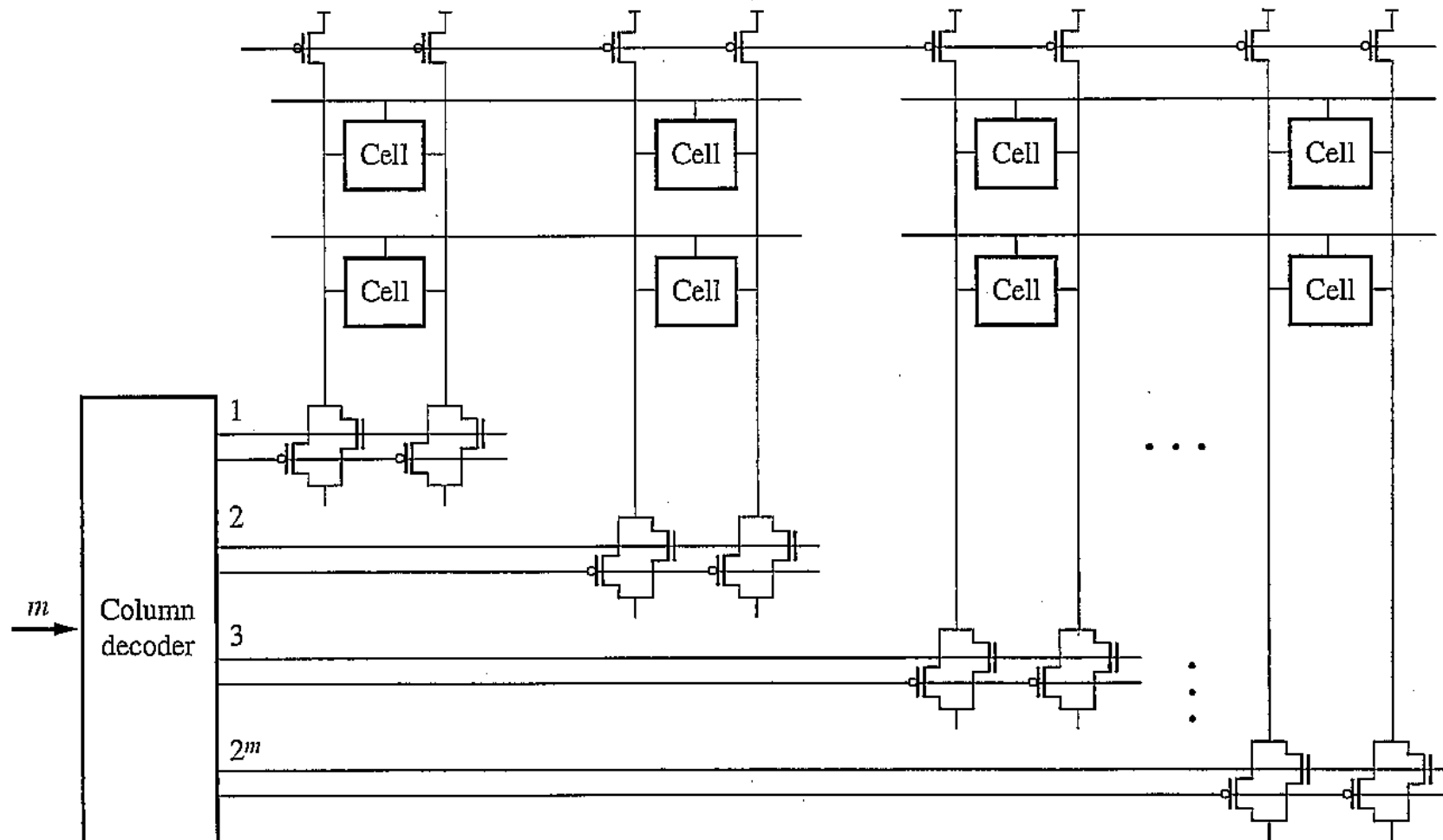


# Column Selection / Read - Write

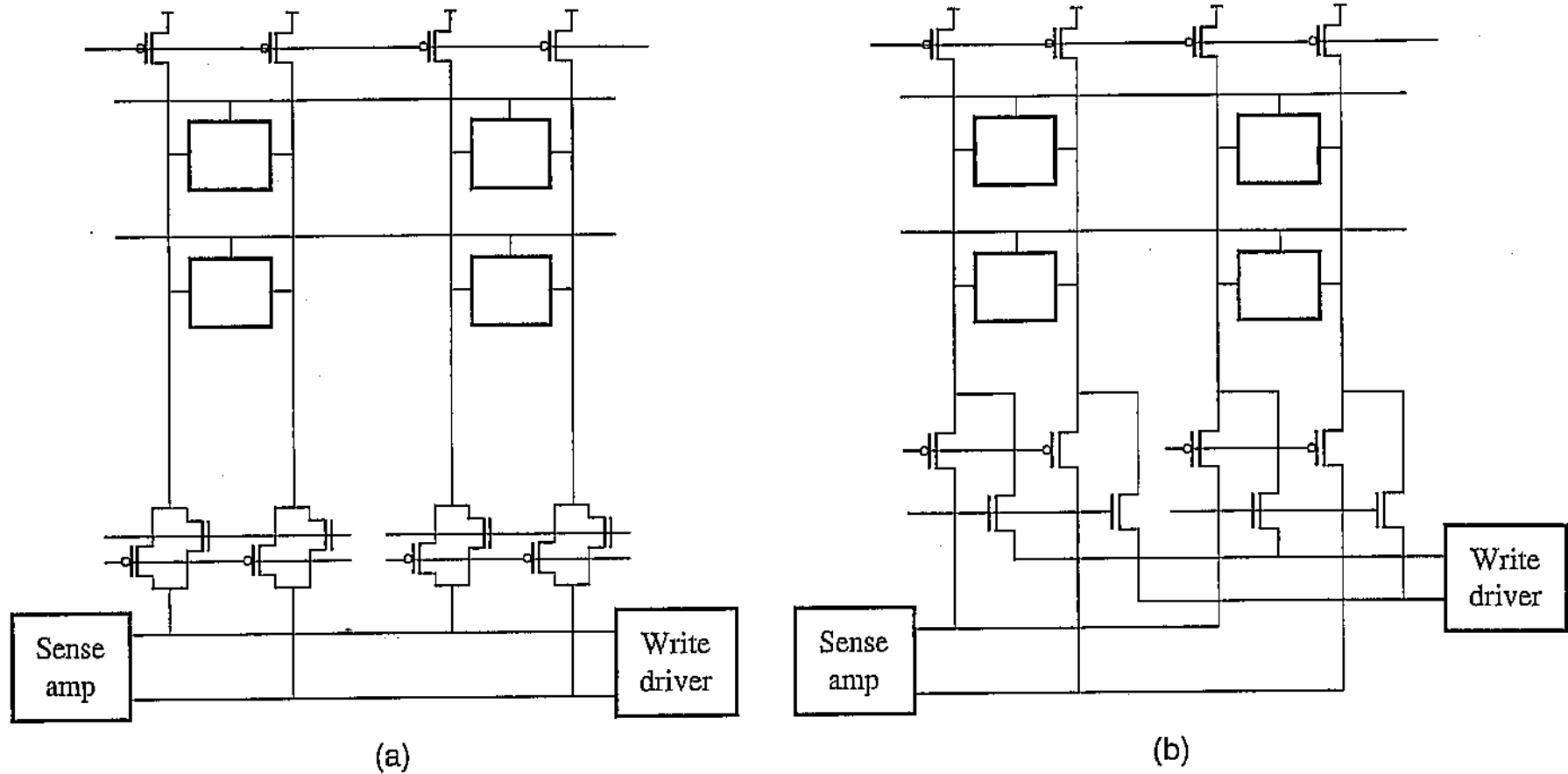


# Tree Decoding Structure



Reduces transistor count

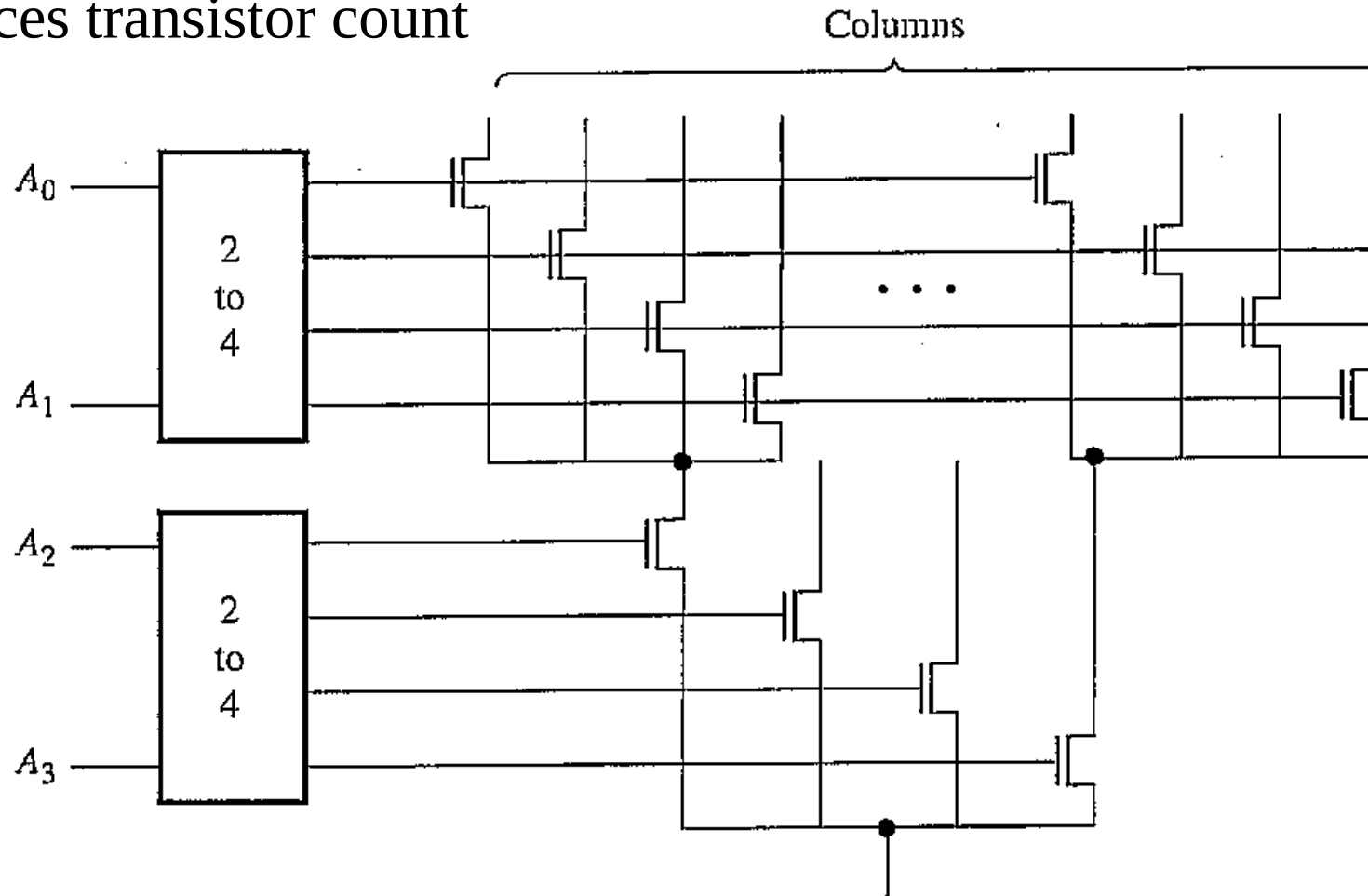


# Write Driver Circuitry

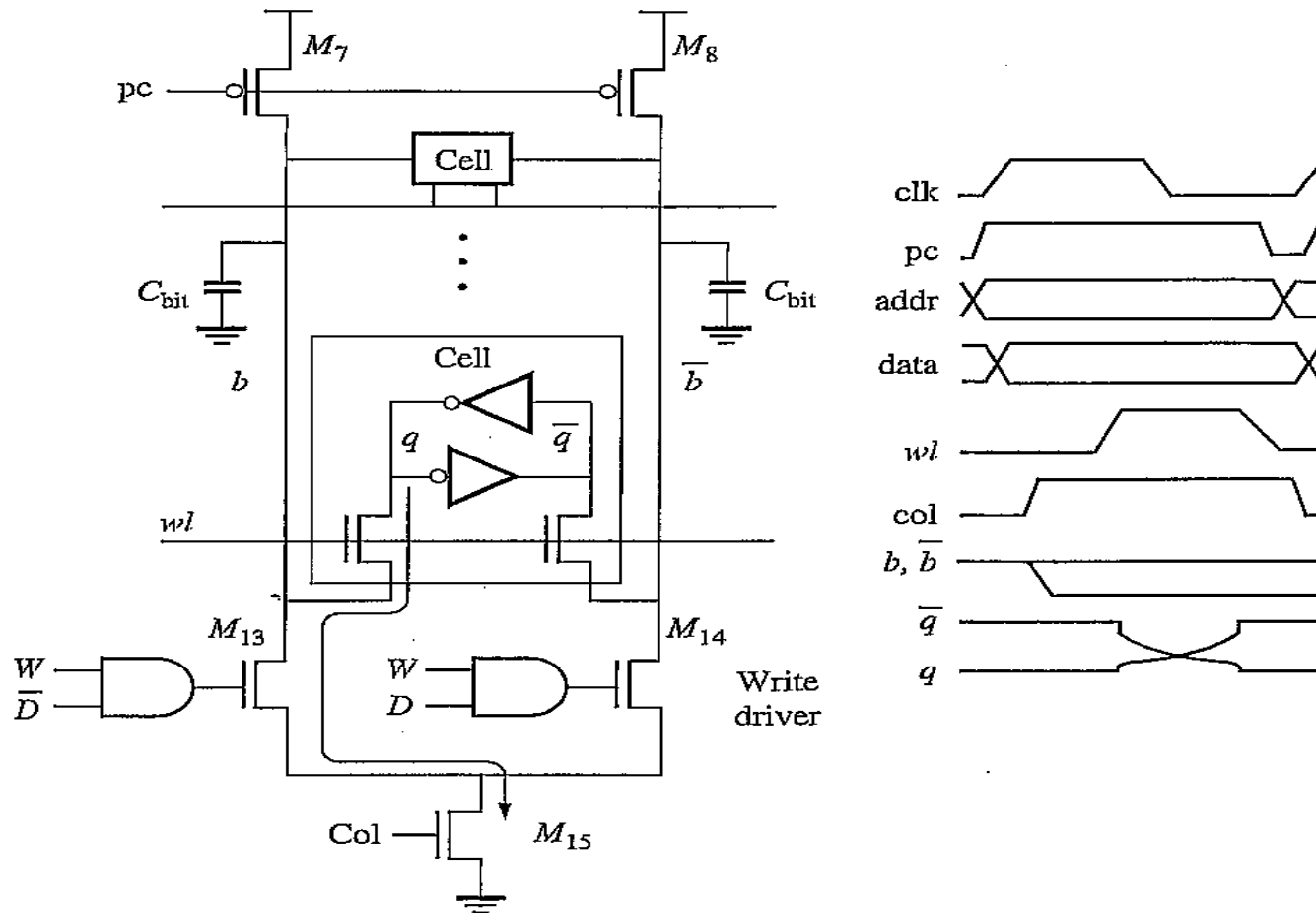

# Basic Read Circuitry

 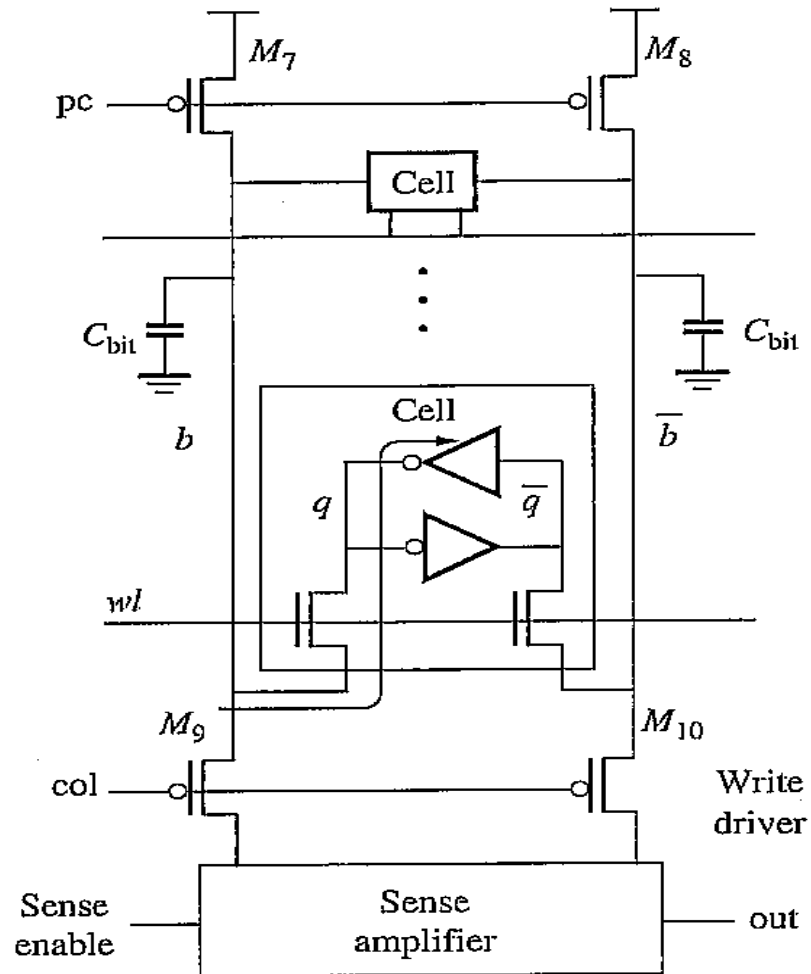

# Differential Voltage Sense Amp

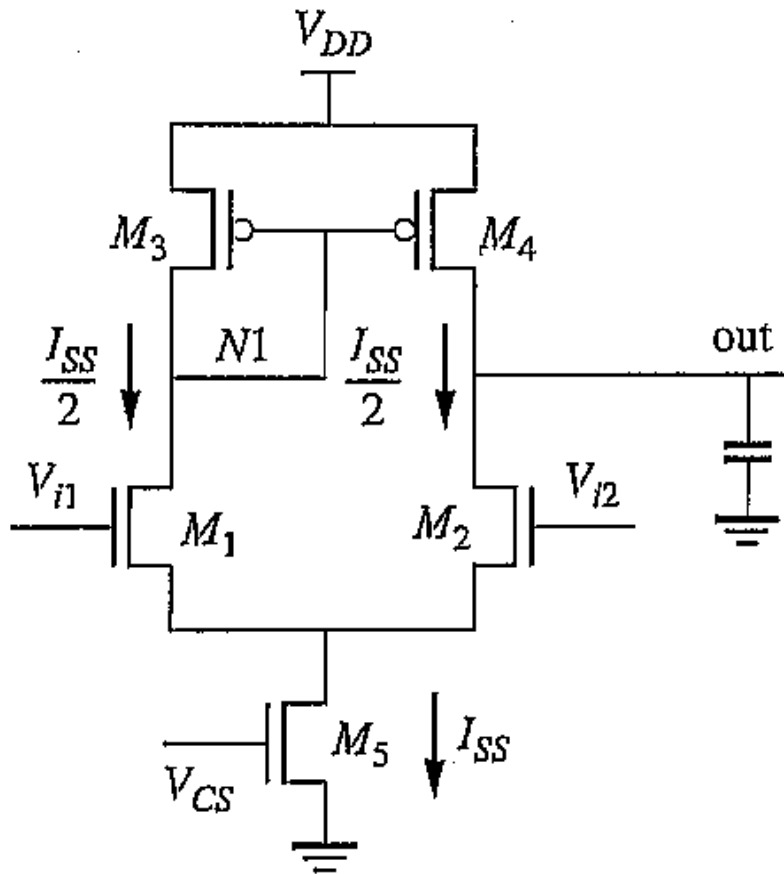


Consists of:

- common source amp
- current mirror
- current biasing


Advantages:

- High Speed Operation
- Good noise immunity
- high CMRR

# Detection of '0' and '1'


 


(a) Discharging output

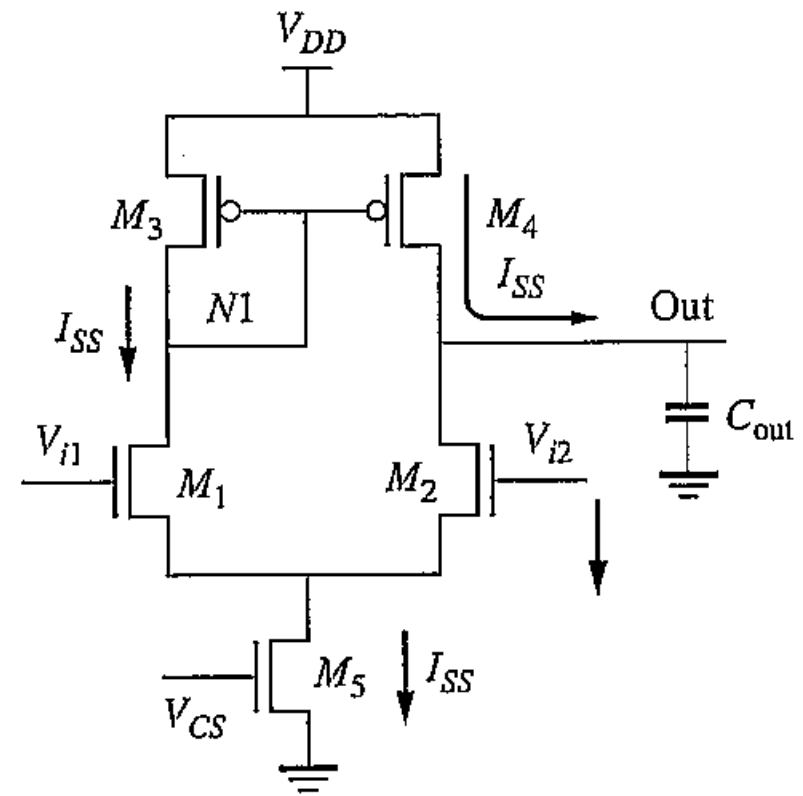

(b) Charging output


# Latch-Based Sense Amp

  




# Memory Architecture


# Basic Memory Architecture

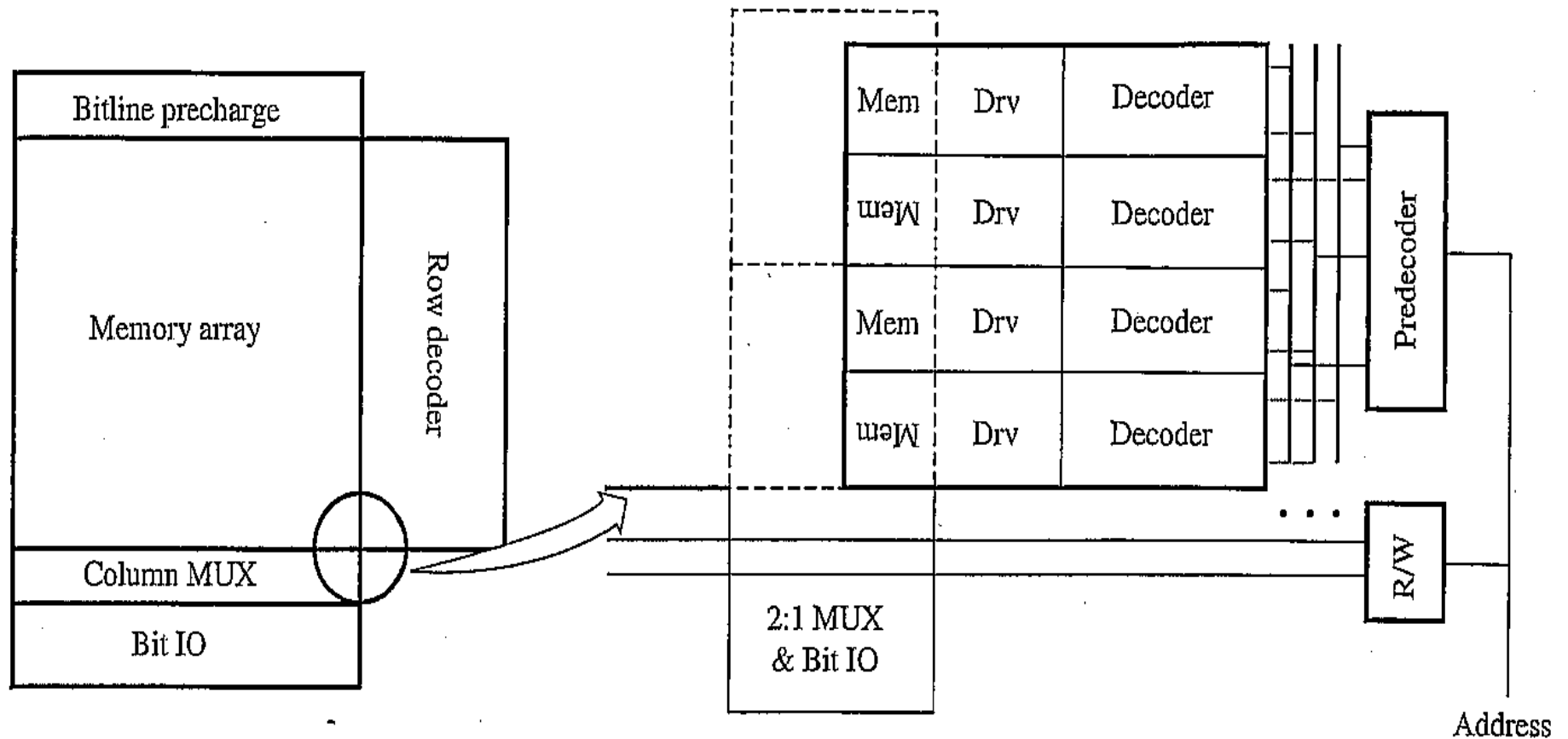

# Partitioning - Divided Wordline

 

# Partitioning – Divided Bitline

 

# Other Memory Families

Content-Addressable Memories      CAM  
Dynamic Random Access Memory   DRAM  
Flash Memory

# Associative Memories

## Content Addressable Memories (CAMs)

Basic architecture is similar to SRAM

Data we seek is associated with a known binary keyword rather than a known binary address


Compare known keyword against previously stored keywords, known as tags, that reference the data we seek

Address decoder → matching scheme


Often used in:

- *cache* memories
- Internet routing tables

# Concept of a CAM Array

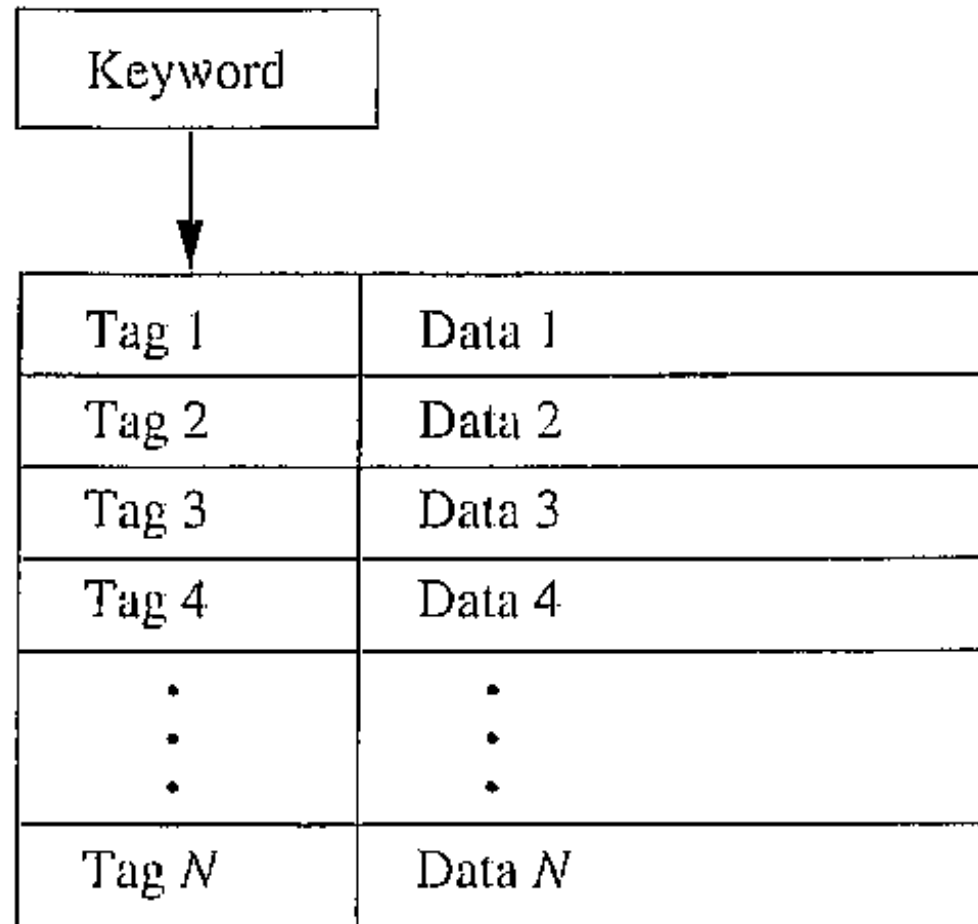


# CAM Lookup Array

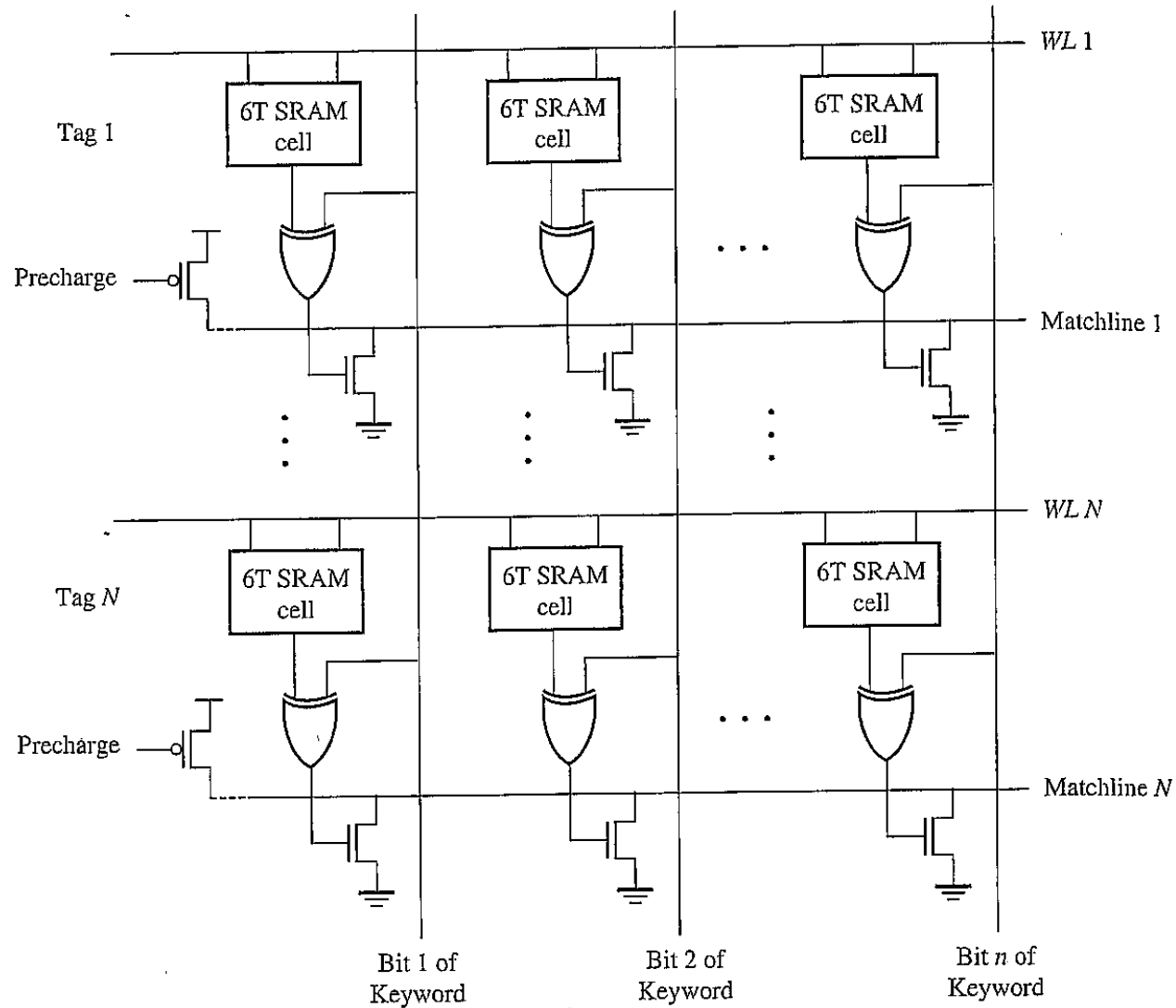




# CAM Memory Cell

 


# CAM Implementation

 


# DRAM


# 1T 1R1C1 DRAM Cell

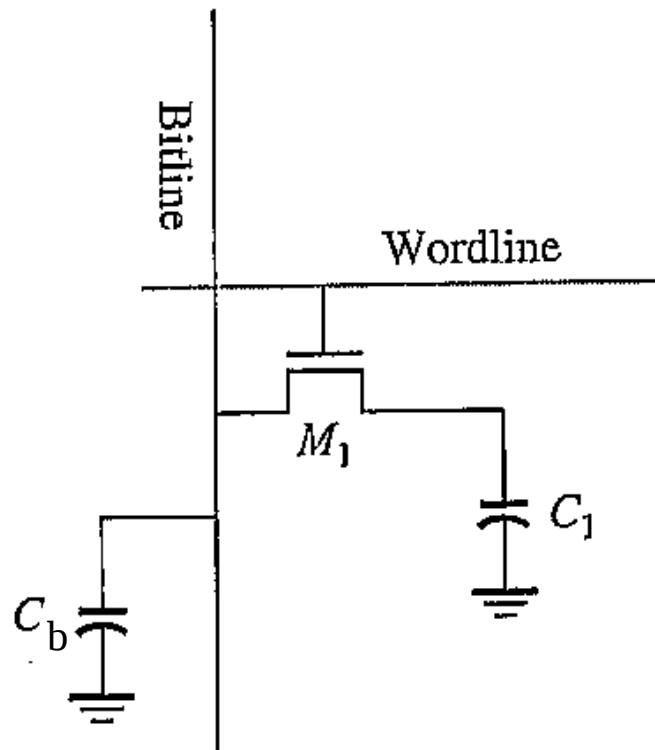


# DRAM Array Configuration

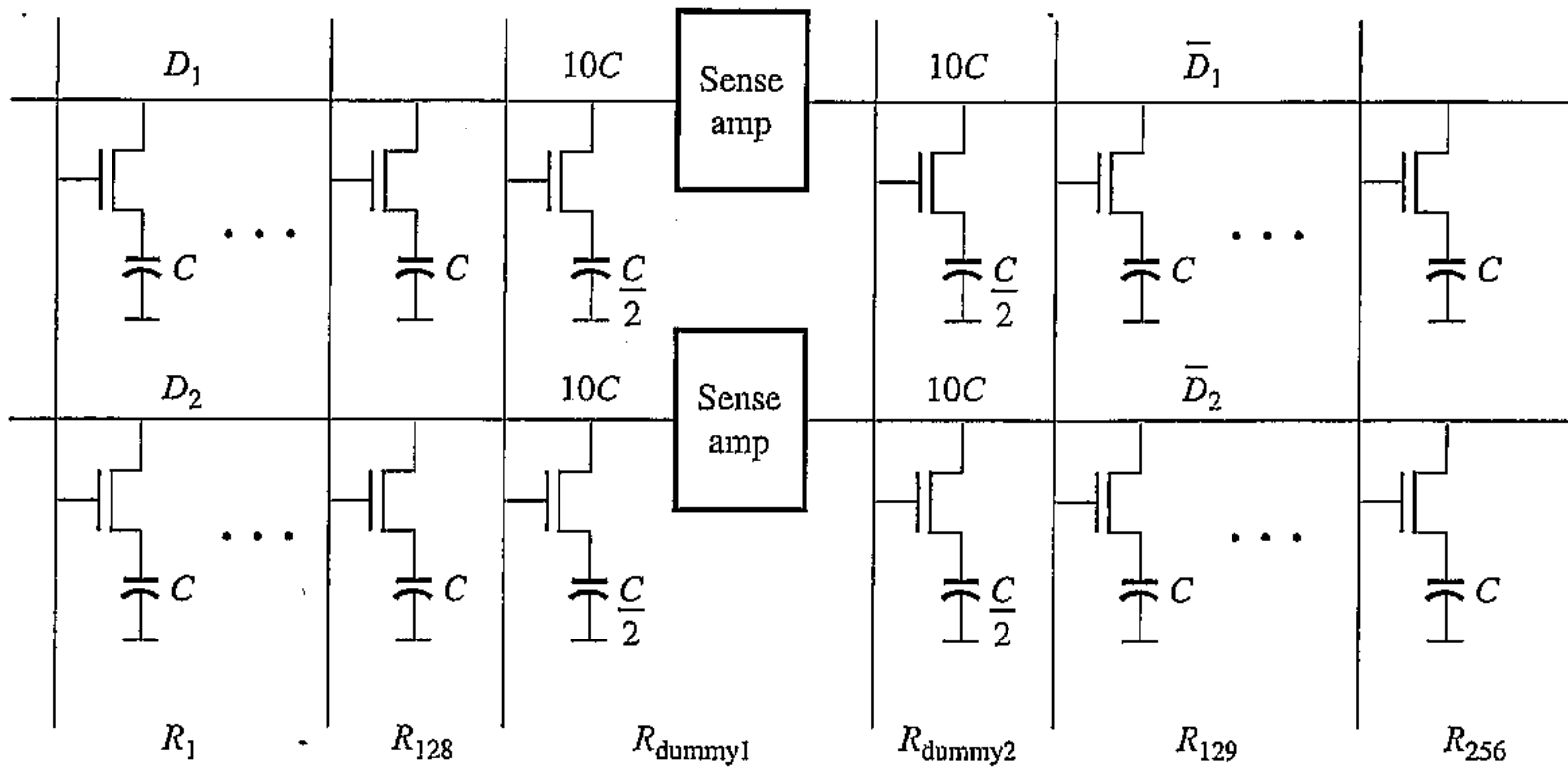

# DRAM Sense/Refresh Circuit

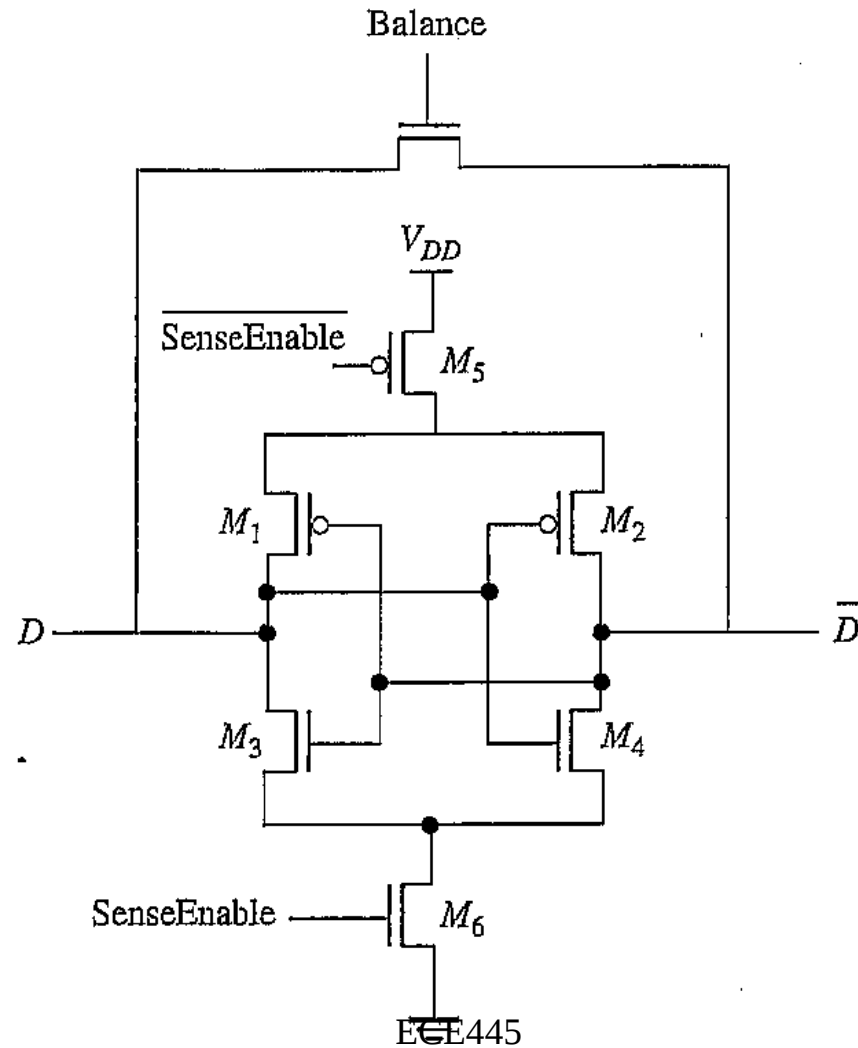

# 64-kbit DRAM – Block Diagram

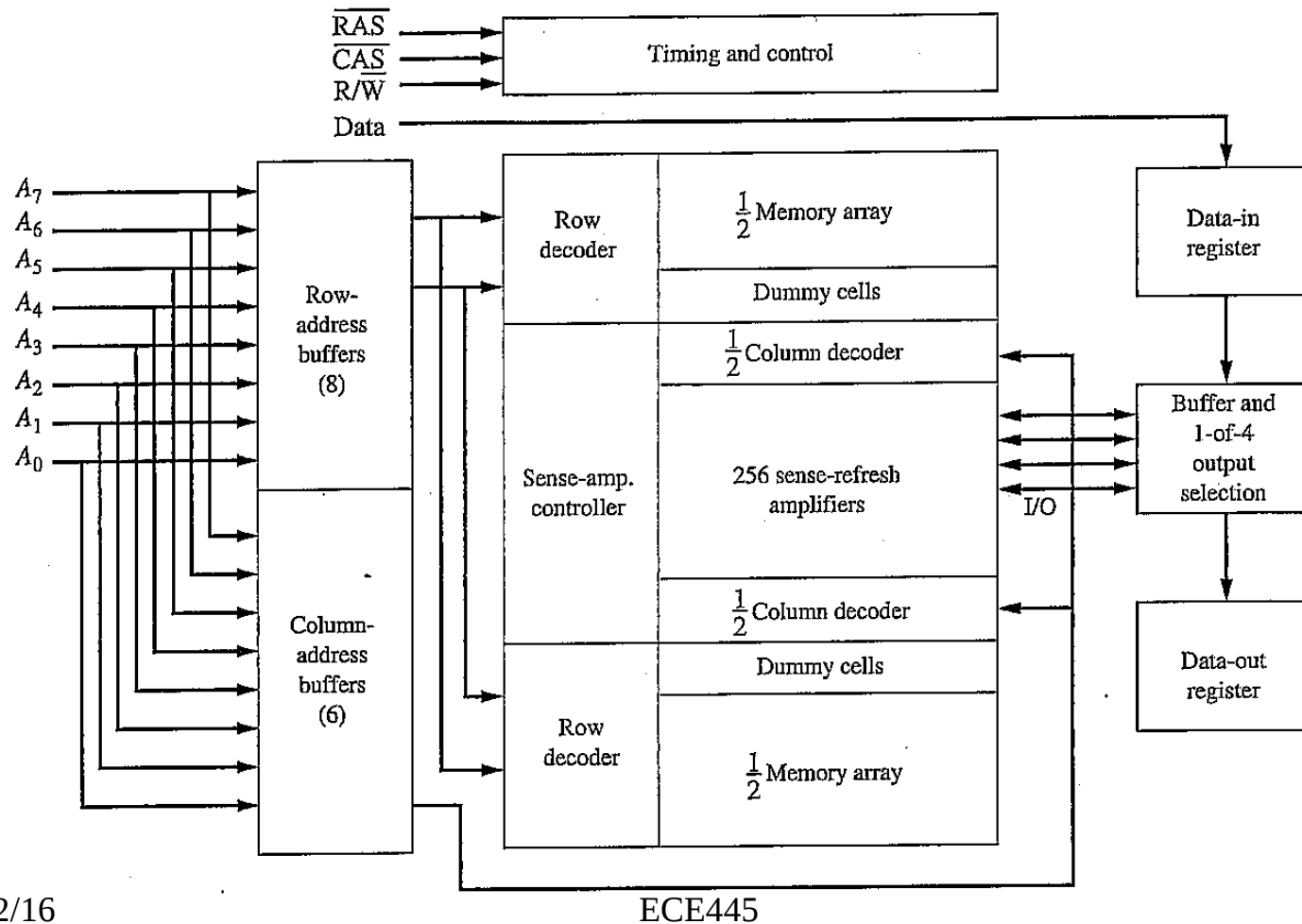

# Flash Memory



# Applications

Read / Write Non-volatile Memory

- USB memory sticks
- Digital cameras
- MP3 players
- ...


$10^6$  R/W operations

1T cell implementation of E<sup>2</sup>PROM


Two architectures

- NAND
- NOR


# Dual-Gate Structure

 

# Schematic Representation

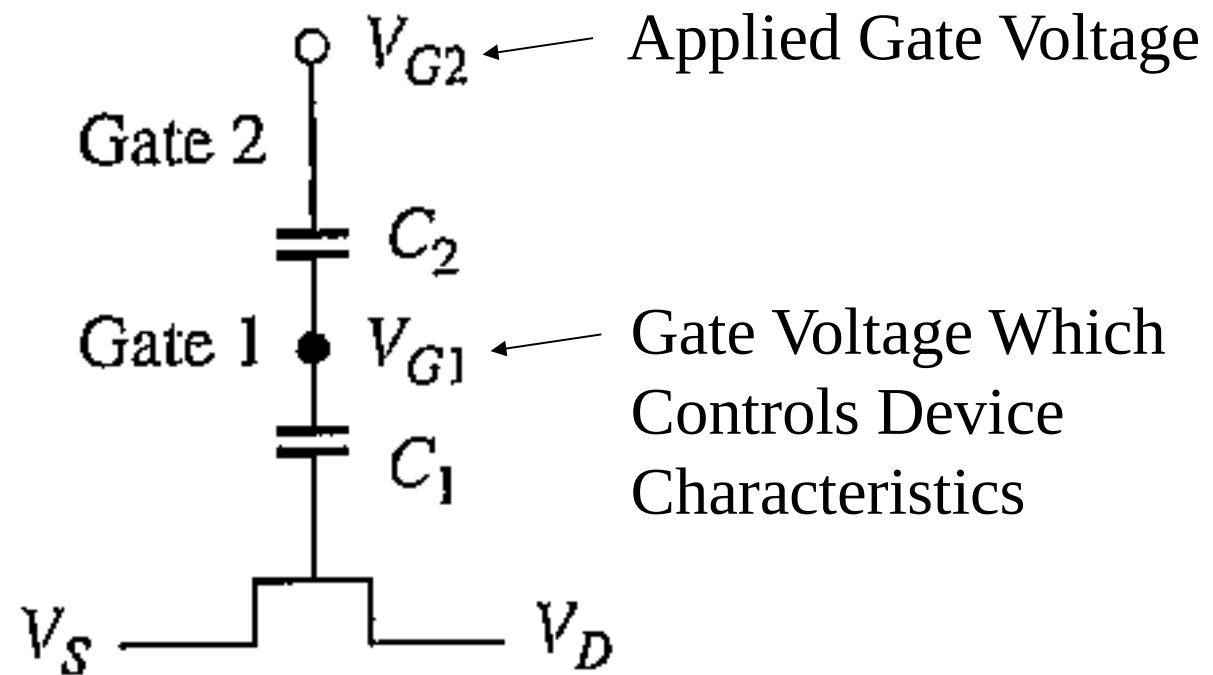


# Capacitive Divider at Gate

 

$$\Delta V_{G1} = \Delta V_{G2} \frac{C_2}{C_1 + C_2}$$

# To Turn The Device On

 


$$V_{G1} > V_t$$

$$\Rightarrow V_{G1} = V_{G2} \frac{C_2}{C_1 + C_2} > V_t$$

$$\Rightarrow V_{G2} > V_t \frac{C_1 + C_2}{C_2}$$


# Device Operation

 

Device operation relies on the ability to store and remove charge from the floating gate  $\rightarrow$  namely node  $V_{G1}$
 
# Write Process

Write process relies on “Hot Carrier Injection” (HCL)




- Raise  $V_{G2}$  and  $V_{DS} \gg V_{DD}$
- Avalanche breakdown of Drain/Substrate Junction
- Electrons are injected through the gate oxide onto the floating gate
- Self-terminating process because  $V_{G1}$  decreases as electrons are injected onto the floating gate


# Example

Assume  $C_1 = C_2 = C$

$V_{DD} = 5V$ ,  $V_T = 1V$

 

(a) Initial state

 


(b) After applying 10 V




# Example

Assume  $C_1 = C_2 = C$

$V_{DD} = 5V$ ,  $V_T = 1V$

 

(a) Initial state

 


(b) After applying 10 V


# Example

Assume  $C_1 = C_2 = C$


$V_{DD} = 5V$ ,  $V_T = 1V$

 

(a) Initial state

 

(b) After applying 10 V

 


(c) After programming

Program by applying  $V_{DS} = 10V$


# Example

Assume  $C_1 = C_2 = C$


$V_{DD} = 5V$ ,  $V_T = 1V$

 

(a) Initial state

 

(b) After applying 10 V

 

(c) After programming


Program by applying  $V_{DS} = 10V$

Assume  $V_{G1}$  drops to 2V


# Example

Assume  $C_1 = C_2 = C$

$V_{DD} = 5V$ ,  $V_T = 1V$

 

(c) After programming

 


Reduce gate voltage  $V_{G2} = 0V$


# Example

Assume  $C_1 = C_2 = C$

$V_{DD} = 5V$ ,  $V_T = 1V$

 

(c) After programming

 


Reduce gate voltage  $V_{G2} = 0V$



# Example

Assume  $C_1 = C_2 = C$

$V_{DD} = 5V$ ,  $V_T = 1V$

 


(c) After programming

  



Raise gate voltage  $V_{G2} = V_{DD}$
 
# Example

Assume  $C_1 = C_2 = C$   
 $V_{DD} = 5V$ ,  $V_T = 1V$




(c) After programming

  

Raise gate voltage  $V_{G2} = V_{DD}$   
 TRANSISTOR IS STILL OFF!!  
 Have written a “1”
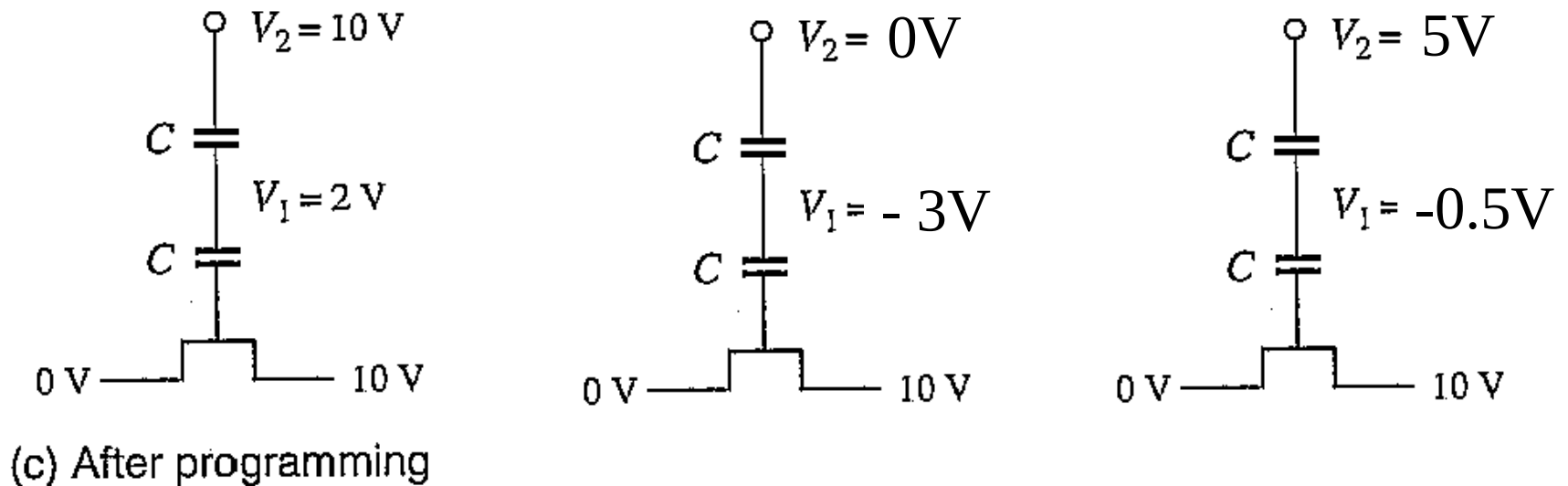
# Example

Assume  $C_1 = C_2 = C$   
 $V_{DD} = 5V$ ,  $V_T = 1V$




Raise gate voltage  $V_{G2} = V_{DD}$   
**TRANSISTOR IS STILL OFF!!**

To turn the transistor on:  $V_{G2} = 8V$



 
# Different Methods to Erase

In a conventional EPROM, UV light is used generate e/h pairs in the  $\text{SiO}_2$  dielectric making the dielectric conductive



(b) Erase process — UV light

# Different Methods to Erase

 


In a E<sup>2</sup>PROM, the charge is removed by “Fowler-Nordheim” (FN) transport.


When the field across the oxide exceed  $\sim 10$  MV/cm, electrons can tunnel across the oxide
 
# Fowler-Nordheim Tunneling


$$j_{\text{FN}} = BE^2 e^{\left(-\frac{b}{E}\right)}$$




# FN Tunneling – 10nm SiO<sub>2</sub>

 


# Symbol

 


# 2T E<sup>2</sup>PROM Cell

 

# 1T Cell - FLASH

 


# NOR Array

 



# Write – “hot carrier injection”

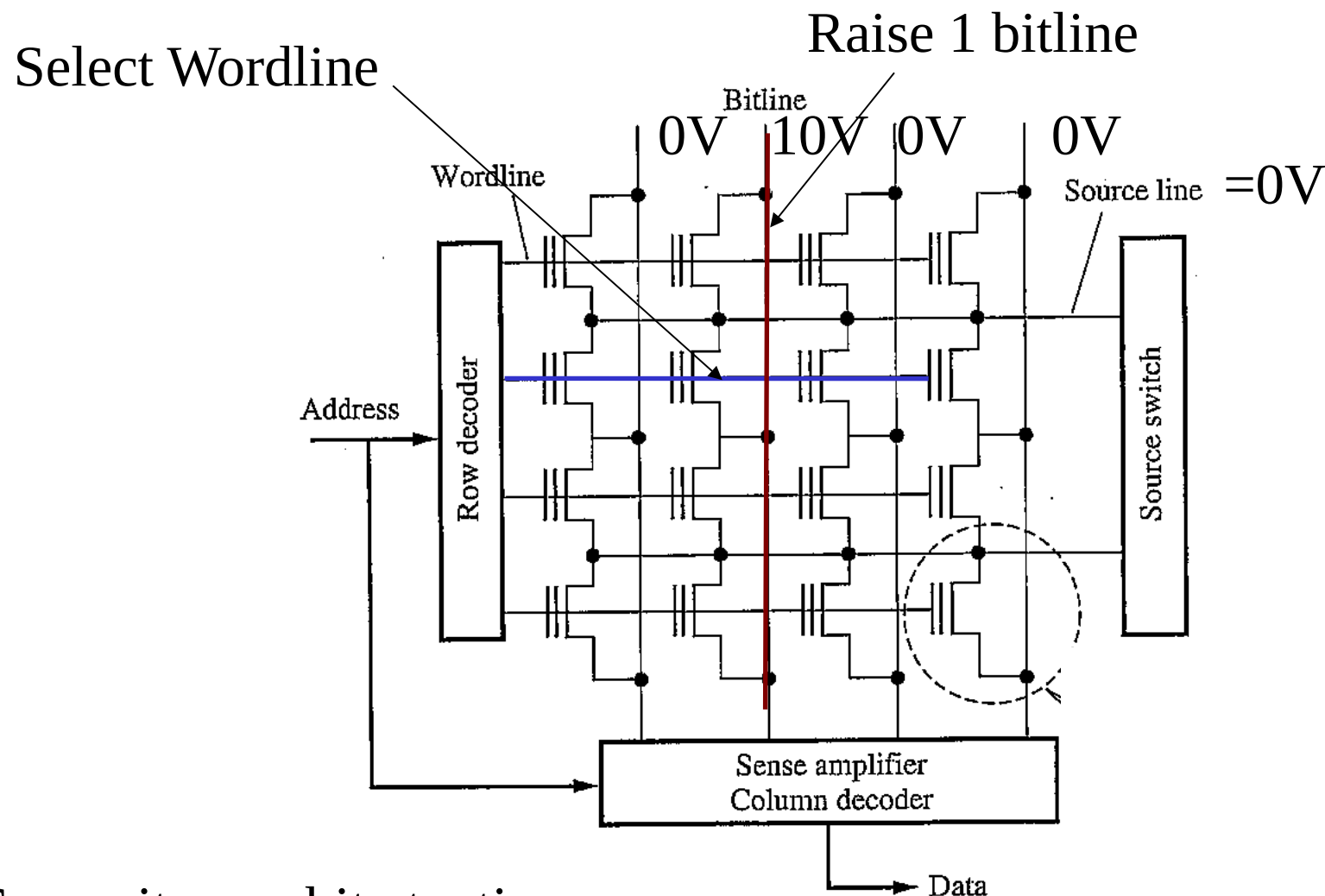

Can write one bit at a time


12/12/16

ECE445

89


# Erase – “Fowler-Nordheim Tunneling”

## 0V on Wordlines

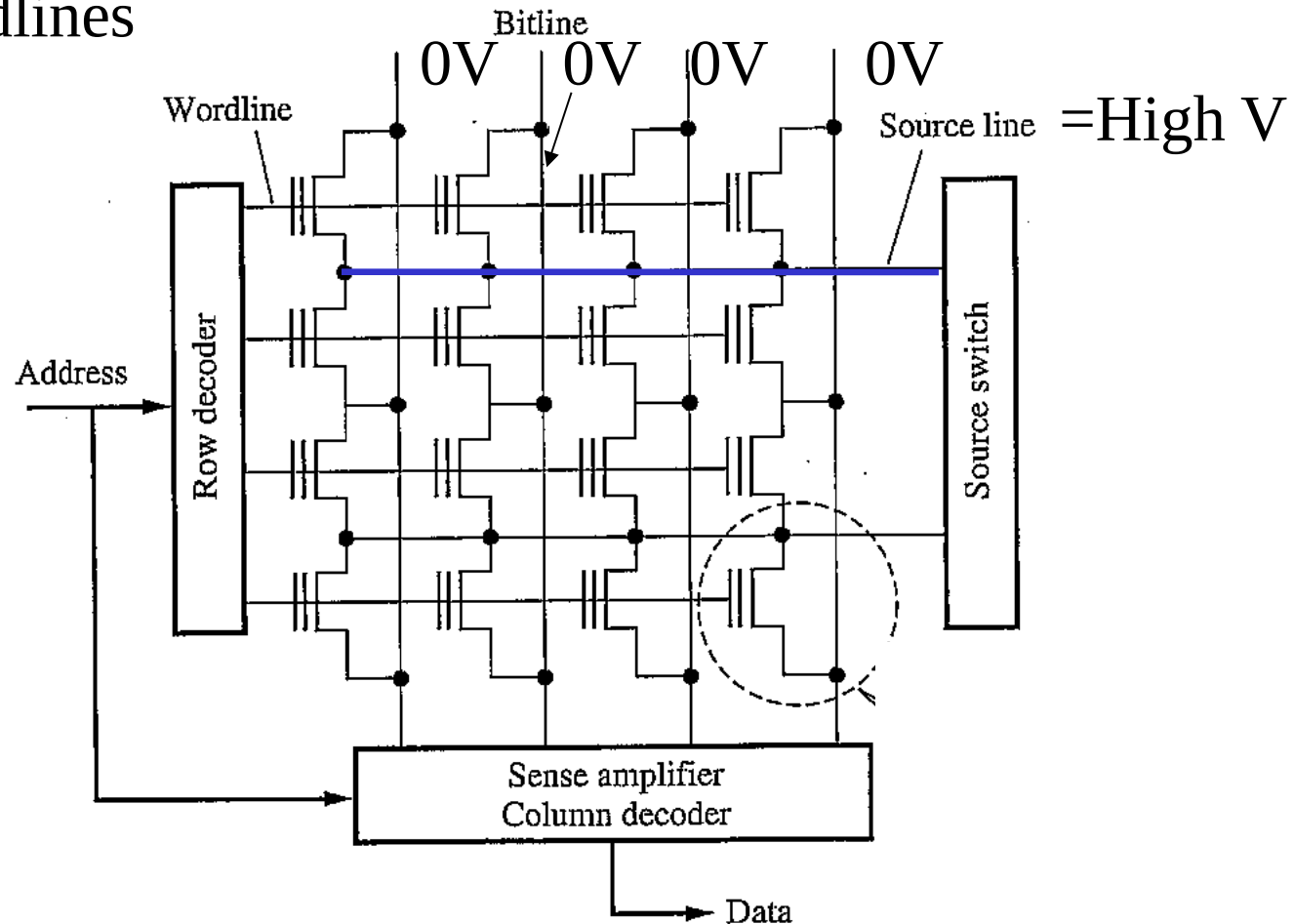



# Erase – “Fowler-Nordheim Tunneling”

0V on Wordlines


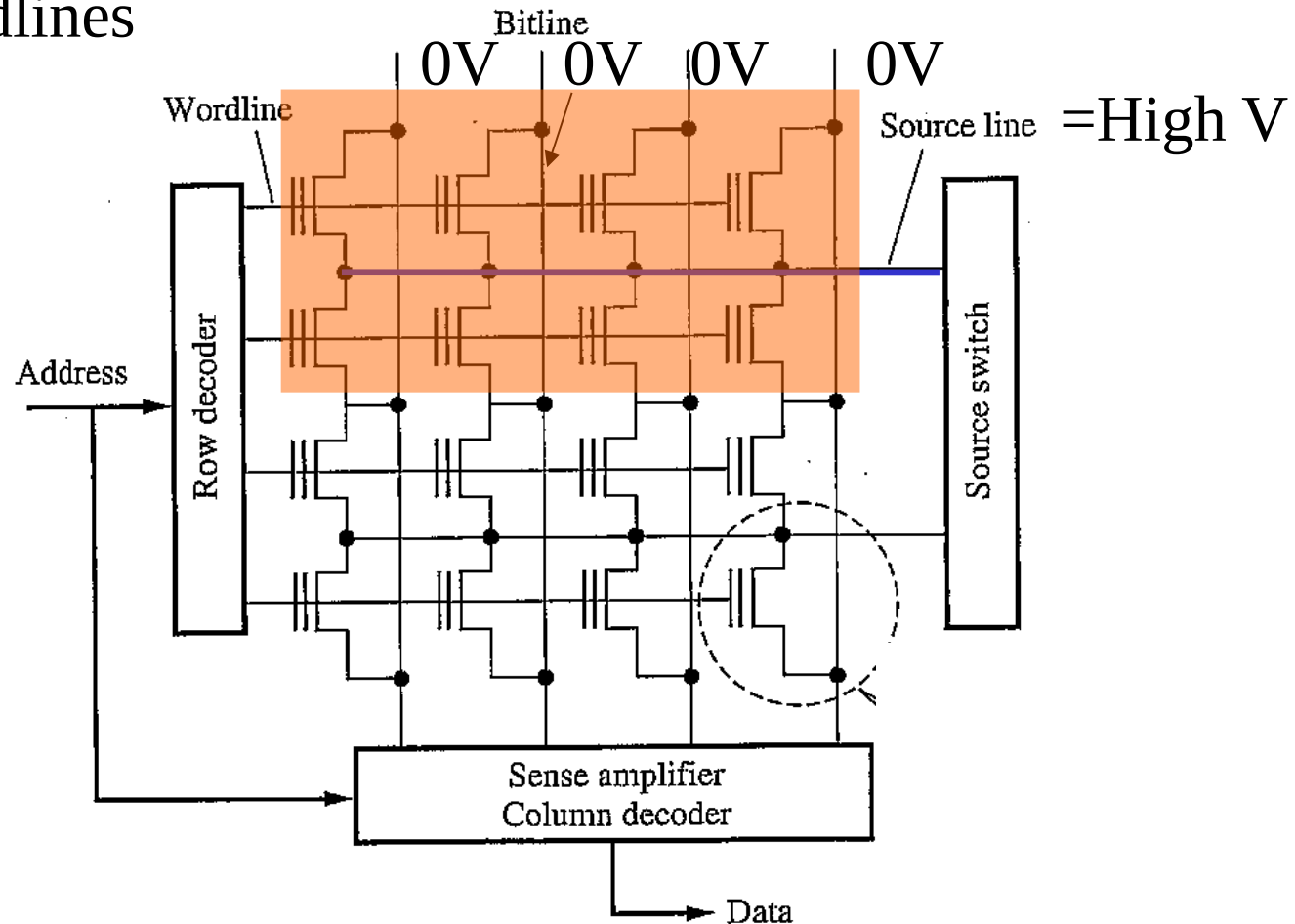


All transistors connected to the source line are erased simultaneously → FLASH

# Write / Erase

 
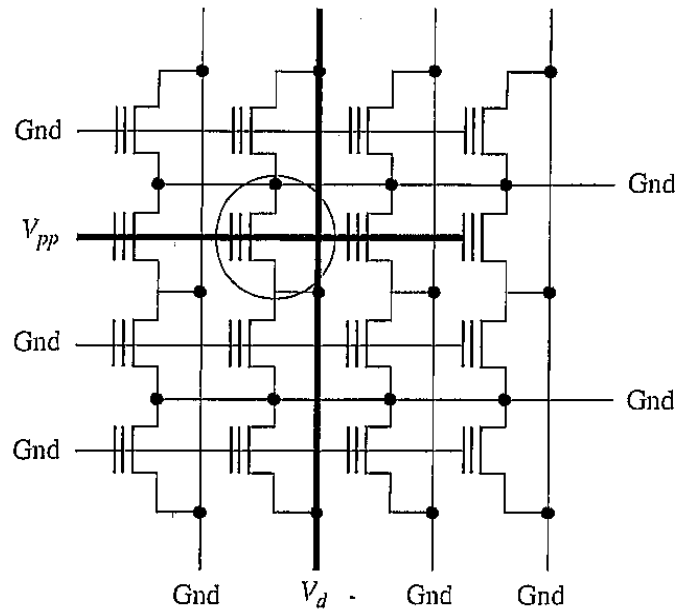


(a) Write operation

  


(b) Erase operation (blockwise only)

# Read Operation

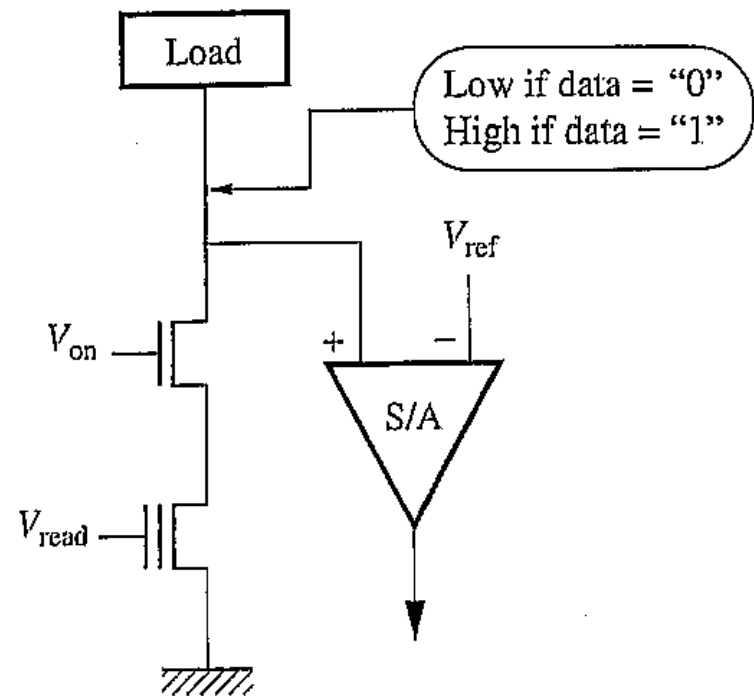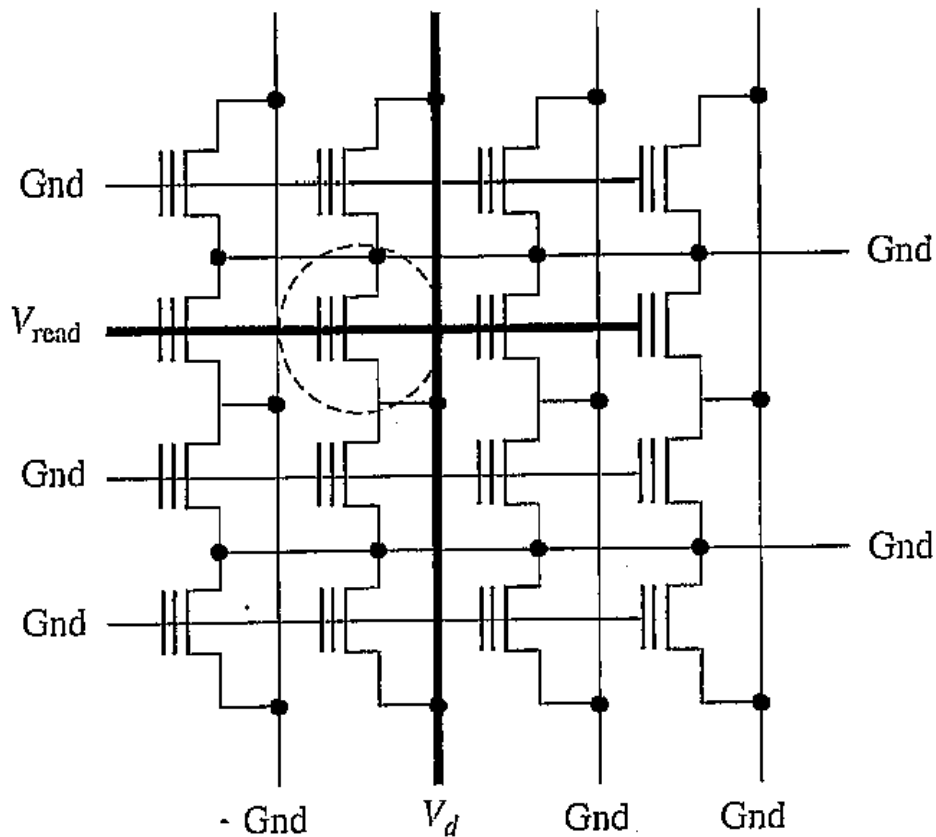

Precharge bitline  
Source line  $\rightarrow$   $Gnd$   
Enable wordline

# NAND Flash Array

 

# NAND vs NOR Arrays

	Write	Read	Erase	Density
NAND	Fast	Slow	Fast	High
NOR	Slow	Fast	Slow	Low

# Issues

Read / Write Endurance

- $> 10^6$  Operations

Redundancy for improved yield

Multi-Bit Cell Architectures – in common practice today!